

# Power Estimation

Sangyoung Park

Chair for Real-Time Computer Systems

Technical University of Munich

[sangyoung.park@tum.de](mailto:sangyoung.park@tum.de)

# Contents

---

- Why power estimation?
- SPICE power analysis
- Power estimation basics
- Signal probability calculation
- Switching Activity
- Leakage Estimation

# Why Power Estimation?

- Two types of control
  - Open loop control
    - Set a control law and expect faithful following
  - Closed loop control
    - Set a control law
    - Read the output
    - Calculate the error
    - Reset the control law
- Purpose of estimation
  - When direct read of the output and/or internal state is not possible
  - Early-stage decision
    - To establish a strategy
    - To figure out potential gain
- Power measurement and estimation are crucial for high-level power saving practices

# How can we estimate power consumption?



- Direct measurement
  - Using lab equipments such as DAQs, oscilloscopes
    - Only for offline characterization
    - Not suitable for final product
  - Using onboard shunt resistors and ADCs
    - Applicable for online usage
    - Uses precious space and resources in the final products
- Indirect estimation
  - Simulation
    - Slow estimation speed
    - Only for offline characterization
  - Estimation using performance parameters
    - Fast enough for online utilization
    - Not all necessary parameters maybe accessible

- SPICE is the de facto standard power analysis tool
  - Simulation program with integrated circuit emphasis
  - A lot of SPICE related literatures and simulators
    - HSPICE, PSpICE, and so on
  - The reference for the higher abstraction levels
  - Accurate but slow
    - Analytical models of MOSFET
- Recently, faster analysis tools were introduced
  - E.g. PowerMill, Spectre, and so on
  - Still accuracy is inferior to SPICE

# SPICE basics

- Solving a large matrix of nodal current using Kirchhoff's Current Law (KCL)
- Primitive elements
  - Resistors, capacitors, inductors, current sources, and voltage sources
- More complex elements
  - Such as diodes and transistors
  - Constructed from the primitive elements
- Analysis modes
  - DC analysis
  - Transient analysis

# SPICE power analysis


- Can estimate all types of power consumption
  - Dynamic/static/leakage
- Not feasible for the entire chip due to the computation complexity
  - Can be used as a characterization tool for higher abstraction level analysis
- Can consider process and other parameter's variation
  - BEST/TYPICAL/WORST

- To speed up the analysis
  - Lose accuracy
- Typical methods
  - Circuit model
    - Approximate the complex equations into a linear equation
  - Tabular transistor model
    - Express the transistor models in tabular forms
  - Switch model
    - Consider a transistors as a two-state switch (on/off)



# Circuit model


- Linear circuit model

 

$$I_{DS} = \frac{k}{2} (2(V_{GS} - V_T)V_{DS} - V_{DS}^2)$$

$$I_{DS} = \frac{k'}{2} (V_{GS} - V_T)^2 (1 + \lambda V_{DS})$$
 
$$I_{DS} = W v_{sat} C_{ox} \frac{(V_{GS} - V_T)^2}{V_{GS} - V_T + E_c L}$$



$$i_{ds} \approx i_0 + g_m v_{gs} + r_{ds}$$

- The linear equation should be numerically evaluated whenever the operating points change

# Tabular transistor model

- Pre-compute a current table
- Look up the table instead of solving an equation
- Table format

$V_{gso}$	$V_{dso}$	$i_{ds}$
0.1	0.1	1
...	...	...
5	5	10

- One-time characterization effort for each MOS
- Event-driven approach can be used for speed-up
- Nearly two orders of magnitude improvement (speed, size)


# Switch model

- RC calculation for timing
- Power is estimated from the switching frequency and capacitance

$$I_{DS} = \frac{k}{2} (2(V_{GS} - V_T)V_{DS} - V_{DS}^2)$$

$$I_{DS} = \frac{k'}{2} (V_{GS} - V_T)^2 (1 + \lambda V_{DS})$$

 
$$I_{DS} = W v_{sat} C_{ox} \frac{(V_{GS} - V_T)^2}{V_{GS} - V_T + E_c L}$$



- Further speed-up, but less accuracy

- Circuit-level power analysis is time consuming
- Need to speed up with reasonable accuracy loss
- Estimation beyond the gate level will be discussed later
- Partially similar to delay characterization
- Dynamic power
  - Capacitive power dissipation
  - Internal switching power dissipation
- Leakage power
  - Accuracy depends on the model of circuit simulation
  - Iterative analytic estimation
  - Simulation based approach

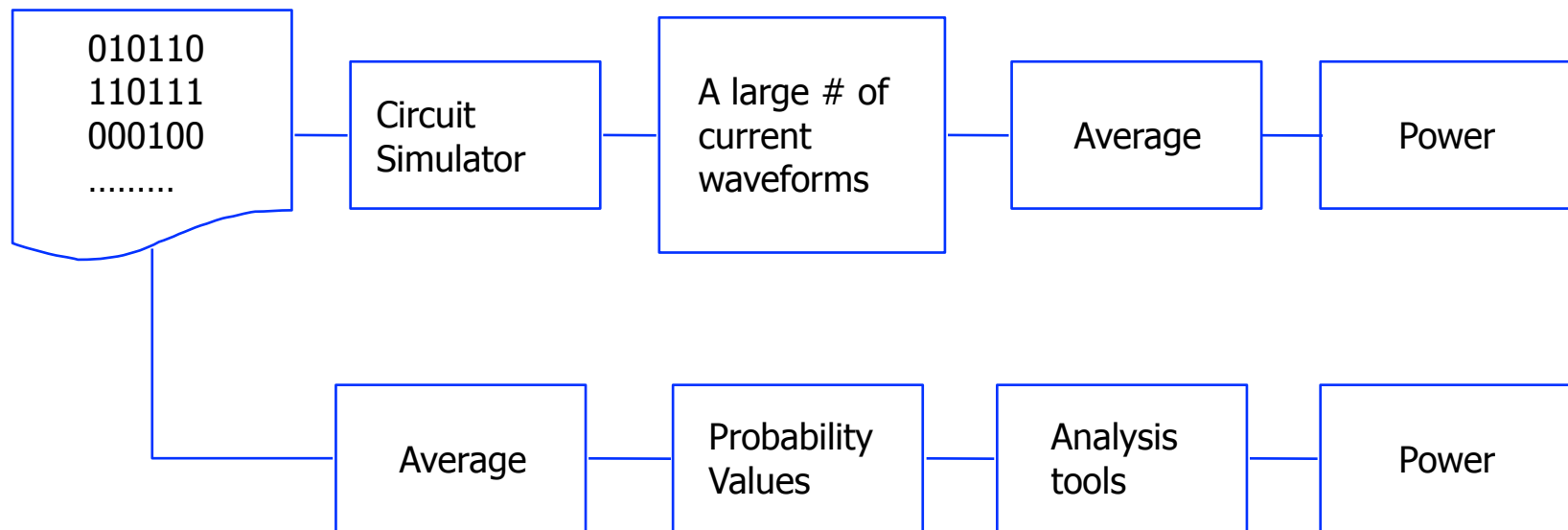- Accuracy vs. speed
  - Too many input patterns → too many simulation runs
  - Too many input patterns → probabilistic analysis



- Parameters
  - Input pattern (logical value)
  - Input slope
  - Output loading capacitance
  - Process condition
- Total # of runs of simulation is the multiplication of the possible number of values of each parameter
  - Some parameters are continuous
    - Input slope, output loading capacitance
    - Piece-wise linear approximation is widely used
  - Process/operation condition
    - BEST/TYPICAL/WORST

# Example: 2-input NAND (I)

- Possible input patterns
  - Dynamic power


💡 Static power

A	B	C	Power
1	r	f	?
1	f	r	?
r	1	f	?
f	1	r	?

A	B	C	Power
0	0	1	?
0	1	1	?
1	0	1	?
1	1	0	?




8 simulation runs!

 

 
# Example: 2-input NAND (II)

- Input slope
  - Depending on the predecessor



 - Capacitance
  - Depending on the successor
  - proportional to the # of fan-outs
  - If we consider four points for capacitance
- Total # of simulation runs for a single input
  - $2 \text{ (rise / fall)} \times 4 \text{ (\# of input slopes)} \times 4 \text{ (\# of capacitance points)}$   
 $= 32 \text{ points}$





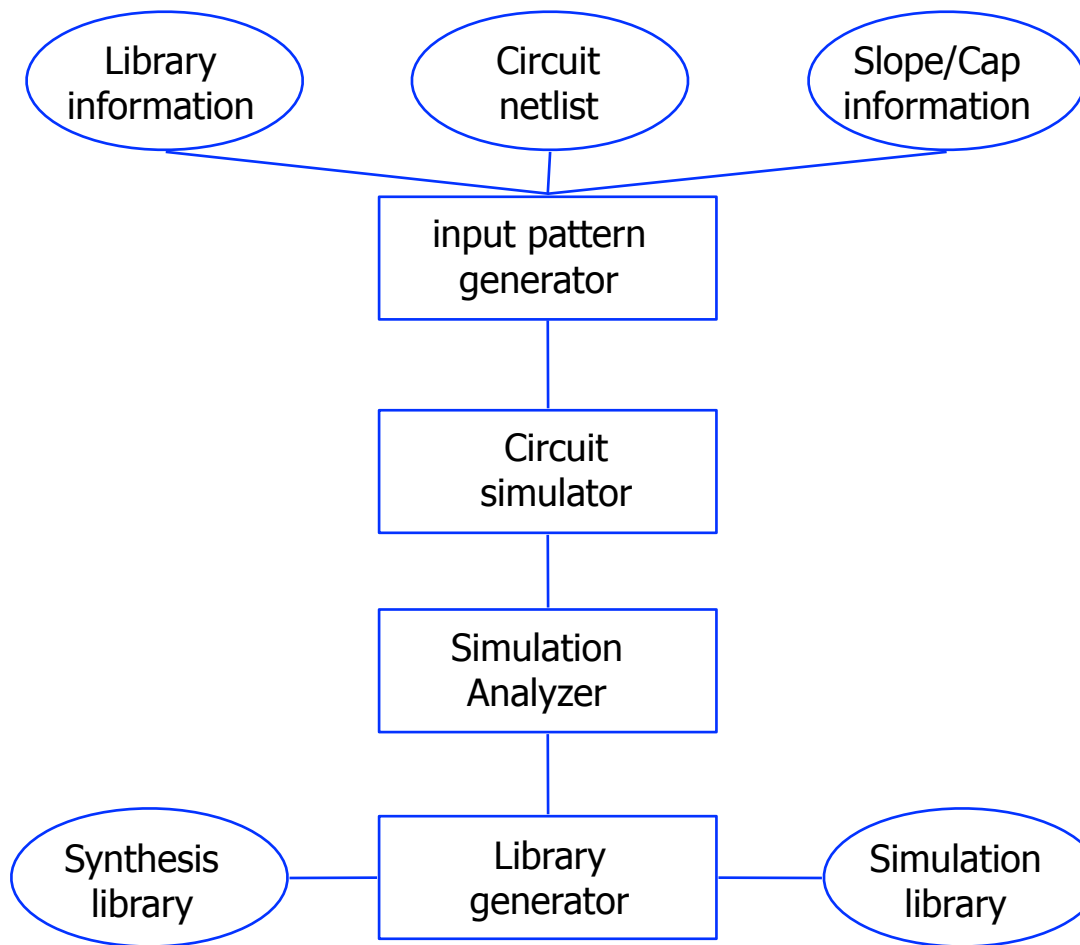
# Example: 2-input NAND (III)

- Process/operation condition
  - Temperature
  - Process variations such as doping density
  - Typically use 3 conditions are widely used
    - BEST/TYPICAL/WORST
- Total # of simulations
  - For dynamic power
    - $(2 \times 2) \times S \times C \times P$
  - For static power
    - $22 \times P$

- Output slope
  - Used as an input slope of the successor
  - Need to know for each simulation point
- Input capacitance
  - Used for computing the total output capacitance of the predecessor
  - Can be estimated by the area of gate (W/L) and  $T_{ox}$
  - Parasitics:  $C_{gs}/C_{gd}$
- All the information should be included in the library



- If we ignore internal capacitance of a logic gate
  - $$P_{avg} = \frac{1}{2} V_{dd}^2 C f$$
- Parameters
  - C: switched capacitance
  - f : the frequency of operation
    - For aperiodic signals: the average # of signal transitions per unit time
    - Called signal activity
- Our concern
  - How to estimate f in a probabilistic manner

# Modeling of signals

- To model the digital signals, need to know
  - Signal probability
  - Signal activity
- $g(t)$ ,  $t \in (-\infty, \infty)$ 
  - A stochastic process that takes the values of logical 0 or 1
  - Transitioning from one to the other at random times
  - SSS: Strict-Sense Stationary
  - Mean ergodic
    - Constant mean with a finite variance
    - $g(t)$  and  $g(t+\tau)$  become uncorrelated as  $\tau \rightarrow \infty$

- Signal probability

$$P(g) = \lim_{T \rightarrow \infty} \frac{1}{2T} \int_{-T}^{+T} g(t) dt$$


- $P(g=1)$  : signal probability

- Signal activity

$$A(g) = \lim_{T \rightarrow \infty} \frac{n_g(T)}{T}$$

- $n_g(t)$ : # of transitions of  $g(t)$  in the time interval between  $-T/2$  and  $+T/2$


- Inverter

 

- AND gate



- OR gate

 

- Assumption

- $g_1, g_2, \dots, g_n$  are independent

- Output signal probability

- Determined by the given boolean function
- NOT: 1 –
- AND: multiply
- OR  $\rightarrow$  NOT ((NOT) AND (NOT))

- By Parker and McClusky
- Algorithm: Compute signal probabilities
  - Input: Signal probabilities of all the inputs to the circuit
  - Output: Signal probabilities of all nodes of the circuit
  - Step1: For each input signal and gate output in the circuit, assign a unique variable
  - Step2: Starting at the inputs and proceeding to the outputs, write the expression for the output of each gate as a function (using standard expressions for each gate type for probability of its output signal in terms of its mutually independent primary input signals)
  - Step3: Suppress all exponents in a given expression to obtain the correct probability for that signal



- Step 3 for protecting reconvergent fanout
  - W/o step 3, the reconvergent fanout node may have a signal probability higher than 1
- A boolean function  $f$


$$P(f) = \sum_{i=1}^p \alpha_i \left( \prod_{k=1}^n P^{m_i,k}(x_k) \right)$$

- $n$ : # of independent inputs
- $p$ : # of products
- $\alpha_i$ : some integer
- Called as the sum of probability products of  $f$
 
# Signal probability calculation: Example

- $y = x_1x_2 + x_1x_3$ ,  $x_i$ ,  $i = 1, 2, 3$  are mutually independent
- $z = x_1x_2' + y$
- $$P(y) = P(x_1x_2) + P(x_1x_3) - P(x_1x_2)P(x_1x_3)$$
$$= P(x_1)P(x_2) + P(x_1)P(x_3) - P(x_1)P(x_2)P(x_3)$$
- $$P(z) = P(x_1x_2') + P(y) - P(x_1x_2')P(y)$$
$$= P(x_1)P'(x_2) + P(x_1)P(x_2) + P(x_1)P(x_3) - P(x_1)P(x_2)p(x_3)$$
$$- P(x_1)P'(x_2)(P(x_1)P(x_2) + P(x_1)P(x_3) - P(x_1)P(x_2)P(x_3))$$
- $P(x_2)P'(x_2) = P(x_2)(1 - P(x_2)) = 0$
- $$P(z) = P(x_1)P'(x_2) + P(x_1)P(x_2) + P(x_1)P(x_3) - P(x_1)P(x_2)p(x_3)$$
$$- P(x_1)P'(x_2)P(x_3)$$

- BDD: Binary Decision Diagram
- Shannon's expansion
  - $f = x_i \cdot f(x_1, \dots, 1, x_{i+1}, \dots, x_n) + \bar{x}_i f(x_1, \dots, 0, x_{i+1}, \dots, x_n)$
- Cofactors w.r.t.  $x_i$  and  $x'_i$ 
  - $f_{x_i} = f(x_1, \dots, 1, x_{i+1}, \dots, x_n)$
  - $f_{\bar{x}_i} = f(x_1, \dots, 0, x_{i+1}, \dots, x_n)$
- Example
  - $f = ab + c$



- $P(f)$ 
  - $P(x_1 \cdot f_{x_1} + \overline{x_1} \cdot f_{x_1}^-)$
  - $P(x_1 \cdot f_{x_1}) + P(\overline{x_1} \cdot f_{x_1}^-)$
  - $P(x_1) \cdot P(f_{x_1}) + P(\overline{x_1}) \cdot P(f_{x_1}^-)$
- A depth first traversal of BDD, with a post order evaluation of  $P(\cdot)$  at every node is required for evaluation of  $P(f)$

# References


- <http://public.itrs.net>
- Gary K. Yeap, “Practical Low Power Digital VLSI Design”, Kluwer Academic Publishers, 1997
- Kaushik Roy and Sharat C. Prasad, “Low Power CMOS VLSI: Circuit Design”, Wiley Interscience, 2000
- Kiat-Seng Yeo, Kaushik Roy, “Low Voltage, Low Power VLSI Subsystems”, McGraw-Hill, 2004

# Switching Activity

- Activity Factor:
  - System clock frequency =  $f$
  - Let  $f_{sw} = \alpha f$ , where  $\alpha$  = activity factor
    - If the signal is a clock,  $\alpha = 1$
    - If the signal switches once per cycle,  $\alpha = 1/2$
    - Dynamic gates: switch either 0 or 2 times per cycle,  $\alpha = 1/2$
    - Static gates: depending on design, but typically  $\alpha = 0.1$
- Switching power:  $P_{sw} = \alpha f V_{DD}^2 C_L$
 
# Switching Activity

- Abnormal switching activity
  - Glitch power
    - Power dissipated in intermediate transitions during the evaluation of the logic function
    - Unbalanced delay paths are principle cause
    - Usually 8% -25% of dynamic power



# Switching Activity

- Transition Probability
  - Dynamic power is data dependent
  - Activity factor is dependent on the run-time data
  - Switching activity,  $P_{0 \rightarrow 1}$ , has two components
    - A static component: function of the logic topology
    - A dynamic component: function of the timing behavior (glitch)
- Static transition probability
  - $P_{0 \rightarrow 1} = P_{\text{out}=0} P_{\text{out}=1} = P_0(1-P_0)$
- With input signal probabilities  $P_{A=1} = 1/2$  and  $P_{B=1} = 1/2$ 
  - NOR static transition probability  
 $= 3/4 \times 1/4 = 3/16$

2-input NOR Gate


A	B	Out
0	0	1
0	1	0
1	0	0
1	1	0



- Transition Probability
  - Switching activity is a strong function of the input signal statistics
  - Generalized switching activity of a 2 input NOR gate
    - $P_{0 \rightarrow 1} = P_0 P_1 = (1 - (1 - P_A)(1 - P_B)) (1 - P_A)(1 - P_B)$


Transition probability for basic gates

	$P_{0 \rightarrow 1} = P_{out=0} \times P_{out=1}$
NOR	$(1 - (1 - P_A)(1 - P_B)) \times (1 - P_A)(1 - P_B)$
OR	$(1 - P_A)(1 - P_B) \times (1 - (1 - P_A)(1 - P_B))$
NAND	$P_A P_B \times (1 - P_A P_B)$
AND	$(1 - P_A P_B) \times P_A P_B$
XOR	$(1 - (P_A + P_B - 2P_A P_B)) \times (P_A + P_B - 2P_A P_B)$

 

Transition probability for 2 input NOR gates

 - Transition Probability
  - Transition probability propagation



- C:  $P_{0 \rightarrow 1} = P_0 P_1 = (1 - P_A) P_A = 1/2 \times 1/2 = 1/4$
- D:  $P_{0 \rightarrow 1} = P_0 P_1 = (1 - P_C P_B) P_C P_B$   
 $= (1 - (1/2 \times 1/2)) \times (1/2 \times 1/2) = 3/16$

# Switching Activity

- Signal Probability (advanced)
  - Generalized switching activity in combinational logic
  - Boolean difference:

$$\frac{\partial f_j}{\partial x_i} = f_j|_{x_i=1} \oplus f_j|_{x_i=0}$$


- Switching activity in sequential logic
- Estimation of glitch power

# Switching Activity

- Decreasing the switching activities
  - No or little performance and/or functional degradation
  - Different coding techniques
    - Fewer bit transitions between two states
  - Boolean expressions simplification
    - Gate minimization
  - Avoid glitches
    - Get rid off unnecessary transitions
  - Power down modes
    - Turn off parts of that are not in use
 
# Switching Activity


- Decreasing the switching activities
  - Example: gray coding
    - Hamming distance of one
    - Used when a sequence is predictable
      - FSMs
      - Address busses
    - Makes full use of the bit-width



# Leakage Estimation

- Transistor leakage estimation
  - Leakage power components
    - Subthreshold leakage is the focus in leakage current modeling

$$I_{\text{subthreshold}} = \frac{\mu W C_{\text{ox}}}{L} V_T^2 e^{\frac{V_{\text{GS}} - |V_{\text{T}}|}{n V_T}} \left( 1 - e^{\frac{-|V_{\text{DS}}|}{V_T}} \right)$$

 

# Leakage Estimation

- Transistors in a circuit
  - Leakage current is strongly dependent on the relative position of on and off devices in a transistor network
- Position of devices
  - If transistors are connected in parallel and turned off, VDS and VS are similar for each other
    - Leakage current can be calculated independently and summed up
  - If transistors are connected in series and turned off
    - Subthreshold current through each transistor must be the same

$$V_{DS_2} = \frac{nkT}{q(1+2\eta+\gamma)} \ln \left( \frac{A_1}{A_2} e^{\frac{\eta V_{DD}}{nkT}} + 1 \right)$$

- Voltage of the I-th transistor

$$V_{DS_i} = \frac{nkT}{q(1+\gamma)} \ln \left( 1 + \frac{A_{i-1}}{A_i} \left( 1 - e^{-\frac{\eta V_{DD}}{nkT}} \right) \right)$$

# Leakage Estimation

- Large-circuit leakage current computation
  - Stack-based leakage estimation
    - On transistors are considered as a short circuit
    - Ignorance of the on resistance of transistors
  - The leakage current of a transistor in parallel with an on transistor is ignored
    - $V_{DS}$  is estimated for the remaining transistors using

$$V_{DS_2} = \frac{nkT}{q(1+2\eta+\gamma)} \ln \left( \frac{A_1}{A_2} e^{\frac{\eta V_{DD}}{nkT}} + 1 \right)$$

- Leakage power

$$V_{DS_i} = \frac{nkT}{q(1+\gamma)} \ln \left( 1 + \frac{A_{i-1}}{A_i} \left( 1 - e^{-\frac{q}{kT} V_{DS_{i-1}}} \right) \right)$$

$$P_{leakage} = \sum_i I_{DS_{q_i}} V_{DS_{q_i}}$$




# Leakage Estimation

- Very large-circuit leakage estimation
- Probabilistic approach
  - Hurdles of large-circuit leakage current calculation
    - Calculation of the leakage current is complicated due to highly nonlinear behavior of the drain current with respect to source/drain voltage
    - SPICE simulation by using nonlinear model is still very expensive
      - Not feasible for the repeated evaluation of large circuits
    - Leakage current of a circuit is highly dependent on the circuit state
      - State probability must be considered
 
# Leakage Estimation

- State probability
  - Three-input NAND SPICE leakage simulation



State (ABC)	Leakage Current (nA)	Leaking Transistors
000	0.095	N1, N2, N3
001	0.195	N1, N2
010	0.195	N1, N3
<b>011</b>	<b>1.874</b>	<b>N1</b>
100	0.185	N2, N3
<b>101</b>	<b>1.220</b>	<b>N2</b>
<b>110</b>	<b>1.140</b>	<b>N3</b>
<b>111</b>	<b>9.410</b>	<b>P1, P2, P3</b>

# Leakage Estimation

- Gate state estimation
  - Necessary to simulate a substantial portion of the gates' states to obtain accurate average leakage of each gate
  - Requires extremely large number of random global circuit vectors
  - Complexity reduction method
    - Probabilistic approach eliminates the need to do simulation over all  $2^n$
    - A small subset of all the possible states is evaluated, based on the notion of dominant-leakage states

# Leakage Estimation

- Calculation of state probability
  - Statistical simulation to measure the average leakage of an entire circuit
    - Monte Carlo experiments
      - In each iteration, a randomly chosen circuit state is applied
  - Probabilistic approach is more effective than statistical simulation for optimization purpose
    - Leakage optimization relies on accurate estimation rather than the estimation of the total leakage

# Leakage Estimation

- Further simplification of the leakage calculation
  - Dominant leakage states
    - Leakage current in some states is significantly smaller than other states
      - A state with more than one off transistor in a path from VDD to GND results in far less leakage than a state with one off transistor (dominant leakage state)
      - A set of dominant leakage states is generally small
    - Example: three-input NAND gate SPICE simulation
      - Average leakage is 1.78925 nA
      - Set of dominant leakage  $D=\{011, 101, 110, 111\}$
      - Only consideration of  $D$ , the average leakage is 1.7055 nA with 4.68% error

- Slides are modified from lecture notes of “Advanced Computer System Design” from Seoul National University (Lecturer: Prof. Naehyuck Chang)