

# Source of Power Consumption

Sangyoung Park

Chair for Real-Time Computer Systems

Technical University of Munich


[sangyoung.park@tum.de](mailto:sangyoung.park@tum.de)

# Contents

---



- CMOS Inverter
- Power and Energy
- Source of Power Consumption
- Dynamic Power
- Static Power
- $(V_{DD}-V_T)$  Design Space
- Total Power Management

 - The CMOS inverter and (b) its representation as a pair of switches operated in a complementary fashion



# CMOS Inverter

- Pull- up and down networks

  


- Static operation
  - Matching for symmetrical transfer characteristic


$$\left(\frac{W}{L}\right)_p = \frac{\mu_n}{\mu_p} \left(\frac{W}{L}\right)_n$$

- $\mu_n$  is 2 to 4 times larger than  $\mu_p$
- Generally devices have the same channel length for a given technology
- Device size:  $(n+p)L^2$  where  $n=1.5$  and  $p=4.5$  for example

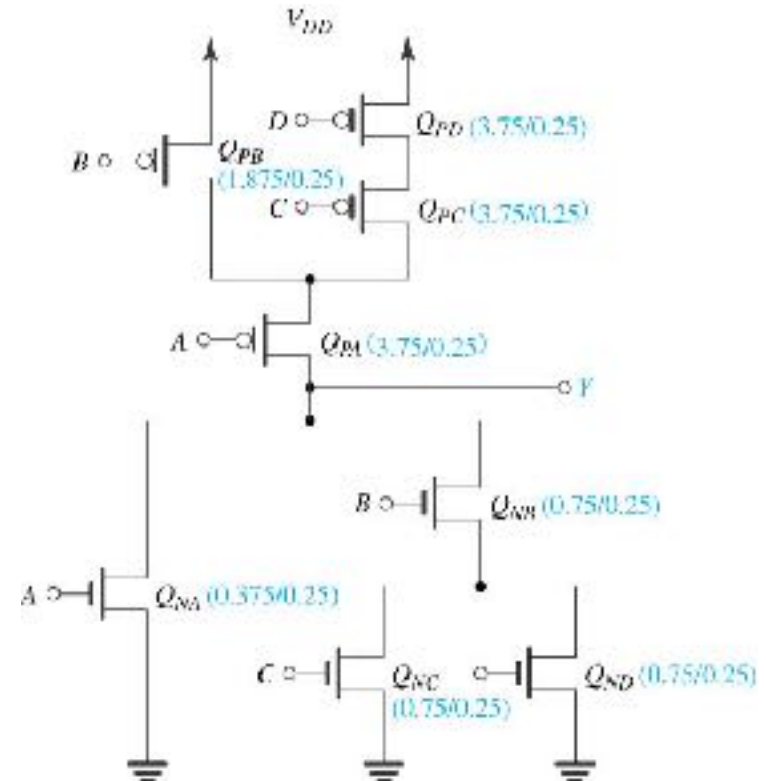- Transistor sizing
  - Determination of the W/L ratio
  - Provide the same current-driving capability in both directions equal to that of the basic inverter



 - Static operation
  - The voltage transfer characteristic (VTC) of the CMOS inverter when  $Q_N$  and  $Q_P$  are matched




$$V_{th} = \frac{V_{DD} - |V_{tp}| + \sqrt{\frac{K_n}{K_p}} V_{in}}{1 + \sqrt{\frac{K_n}{K_p}}}$$

$$k_n = k'_n \left( \frac{W}{L} \right)_n$$

$$k_p = k'_p \left( \frac{W}{L} \right)_p$$

 
- Definitions of propagation delays and switching times of the logic inverter





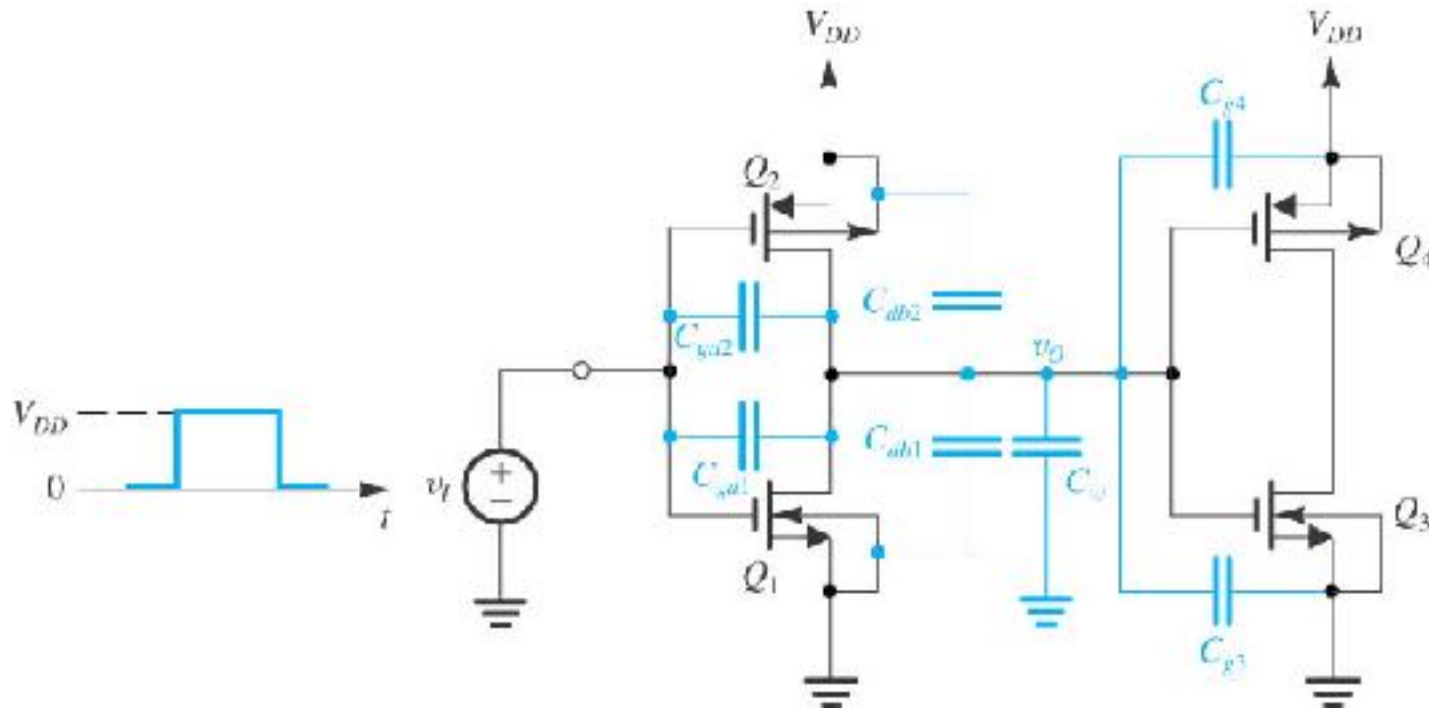
# CMOS Inverter

- Dynamic operation
  - Parasitic capacitance



 
# CMOS Inverter

- Dynamic operation
  - Low to high transition



- High to low transition

 

# Power and Energy

- Power consumption of digital circuits is defined by the supply voltage times the current flow from  $V_{DD}$  to GND
  - Generally,  $V_{DD}$  is constant and  $I_{DD}$  is variable
- Instantaneous power:  $P(t) = I_{DD}(t)V_{DD}$
- Energy:  $E(T) = \int_0^T P(t)dt$
- Average power:  $\overline{P(T)} = \frac{E(T)}{T}$

- Dynamic power
  - Current flow from  $V_{DD}$  to GND when logic transition occurs
    - Switching power
    - Short-circuit power
    - Glitch power
- Static power
  - Current flow from  $V_{DD}$  to GND regardless of logic transition
    - DC current
    - Leakage power

- Traditional CMOS circuits
  - Slow operation
    - Negligible dynamic power consumption
    - Electric watches, calculators, etc.
  - High  $V_{DD}$  and high  $V_T$ 
    - Negligible leakage power consumption
    - Small short-circuit current
- Modern high-speed CMOS
  - Fast operation
    - High dynamic power
  - Low  $V_{DD}$  and low  $V_T$ 
    - Less dynamic power but more leakage power per unit transistor
  - Power is the most important design constraints
    - Large-scale integration and thus power per unit area increase dramatically


# Dynamic Power

- Switching power

$$P(t) = \frac{dE}{dt} = V_{DD} \times I_{DD}(t)$$

- A step voltage is applied at  $t=0$

$$i_{DD}(t) = C_L \frac{dV_0}{dt}$$

 


- Energy transferred from the power supply

$$E_{01} = \int_0^{t_d} P(t) dt = V_{DD} C_L \int_0^V dV_0 = C_L V_{DD} V$$

# Dynamic Power
 
## – Switching power

- When  $V = V_{DD}$ ,  $E_{0 \rightarrow 1} = C_L V_{DD}^2$
- $C_L V_{DD}^2 / 2$  is dissipated by heat
- $C_L V_{DD}^2 / 2$  is stored in the capacitor
- The remaining  $C_L V_{DD}^2 / 2$  is dissipated by heat again when high-to-low transition occurs
- High-to-low transition does not draw additional current from the power supply





# Dynamic Power

- Switching power:

$$P_{sw} = f_{sw} V_{DD}^2 C_L$$

$$E_{tot} = V_{DD} Q = V_{DD} C_L \Delta V = \frac{C_L C_{int}}{C_L + C_{int}} V_{DD}^2 = (C_L || C_{int}) V_{DD}^2$$

  



# Dynamic Power

- Gate capacitance

$$C_g = C_{sg} + C_{dg} + C_{bg}$$

- $C_{gb}$  : sum of the gate-to-bulk capacitances


- Overlap capacitance

$$C_{ov} = C_{dg1} + C_{dg2} + C_{dg3} + C_{dg4} + C_{sg3} + C_{sg4}$$

- Due to Miller effect:  $C_{dg1} = C_{dg2} = 2C_{ox}x + dW$
- $C_{dg3} = C_{dg4} = C_{sg3} = C_{sg4} = C_{ox}x + dW$


- Diffusion capacitance

- Interconnect capacitance

 


 
# Dynamic Power

- Reduced swing switching power
  - Rail-to-rail swing:  $V_{DD}$  to GND
  - When  $V_{OH} < V_{DD}$ , swing is  $V_{OH}$  to GND
  - Reduced bit-line in memory


  
# Dynamic Power

- Short-circuit power
  - Transient current from VDD to GND when logic transition occurs



# Dynamic Power

## – Short-circuit power

when assuming  $V_{thn} = V_{thp} = V_{th}$


device parameter  $\beta_n = \beta_p = \mu C_{ox} \frac{W}{L}$

$\mu$ : carrier mobility

$C_{ox}$ : Oxide capacitance

$\tau$ : rise and fall time

 
$$P_{sc} = \frac{\mu C_{ox} W}{12 L} (V_{DD} - 2V_{th})^3 \tau f$$



# Dynamic Power

- Impact of load capacitance
  - As output loading increases:


Current envelope	width	peak	integration
$i_{\text{short}}$	no change	decrease	decrease
$i_c$	increase	increase	increase
$i_{\text{short}} + i_c$	increase	increase	increase

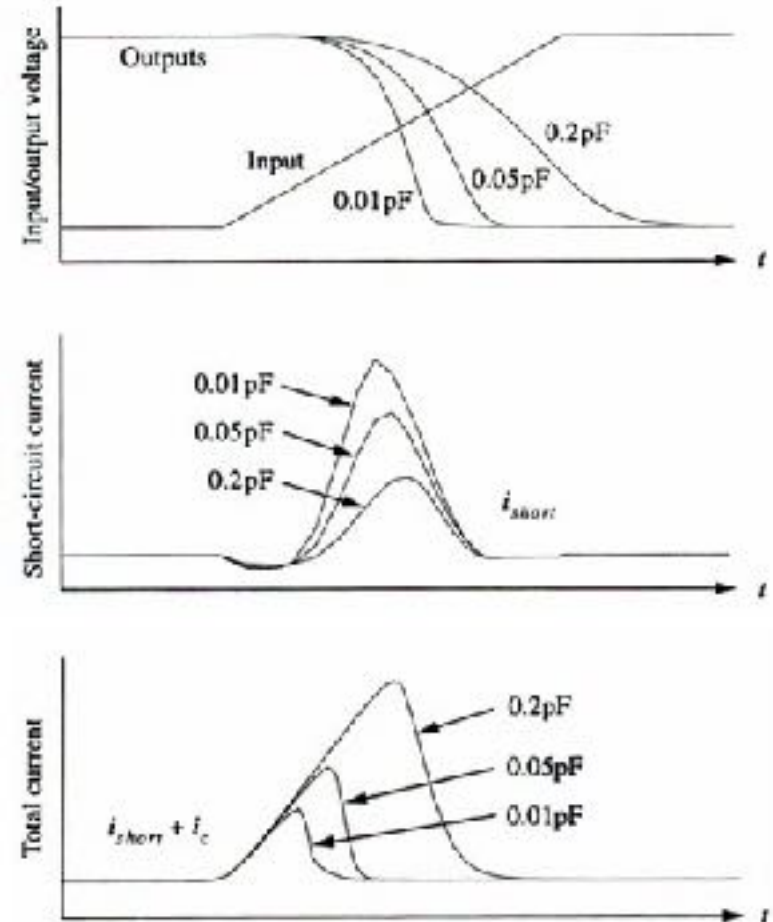

# Dynamic Power


- Impact of input slope
  - As input signal slope deteriorates:

Current envelope	width	peak	integration
$i_{\text{short}}$	increase	increase	increase
$i_c$	increase	decrease	no change
$i_{\text{short}} + i_c$	increase	decrease	increase

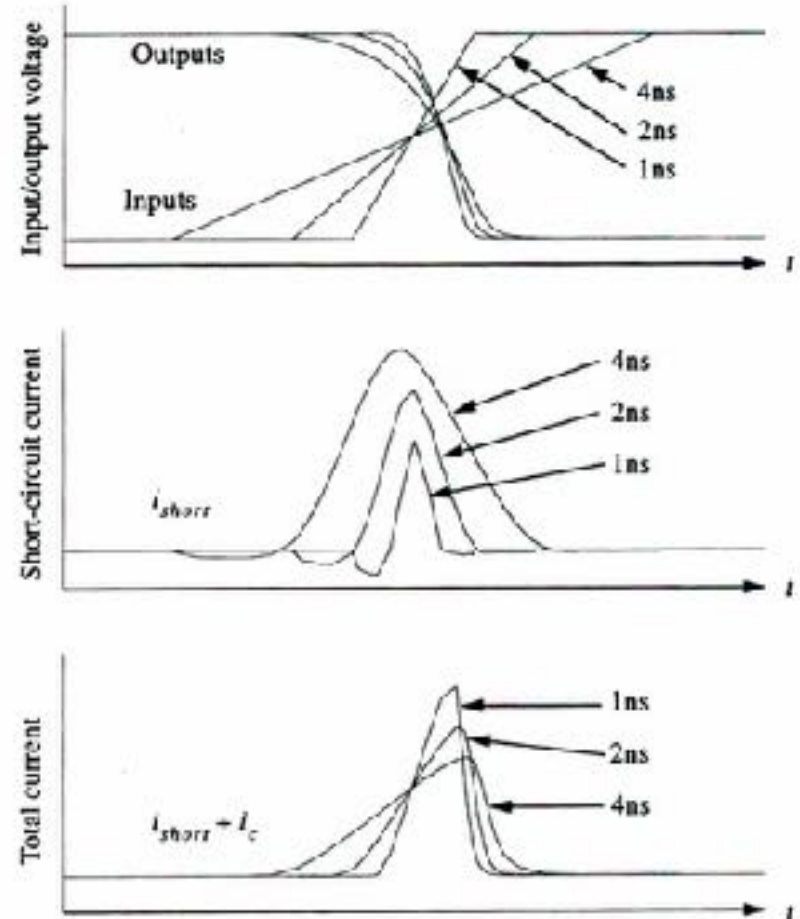


# Static Power

- DC current
  - Pseudo NMOS logic

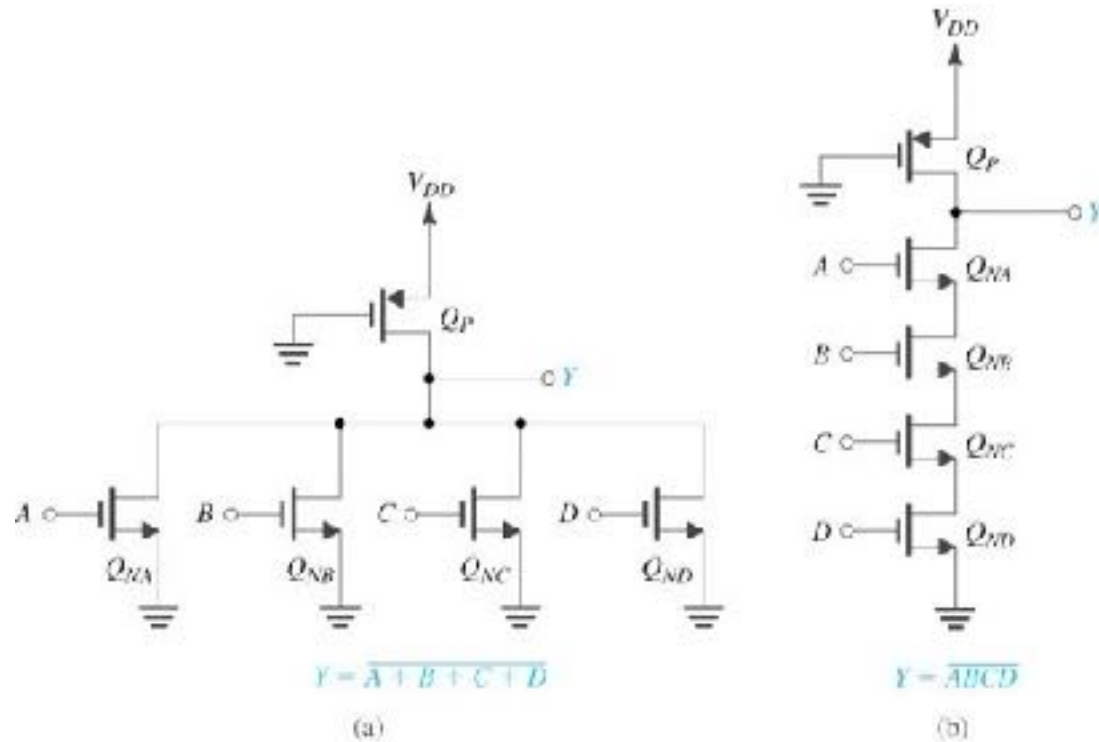

 - DC current
  - Steady current flow from VDD to GND
  - Either logic value is 0 or 1 depending on the logic structure
    - Mostly when the output is 0






# Static Power

- Leakage current
  - A transistor switch is a resistive-capacitive network between the power supply and GND
  - Non-ideal off-state characteristics (a finite resistance) makes current draw even when the transistor is in the cut-off state

## – Leakage current overview


- If channel is locking:
  - Subthreshold current ( $I_{\text{subth}}$ )  $\leq 180\text{nm}$
  - Gate tunneling to S/D ( $I_{\text{gate}}$ )  $\leq 90\text{nm}$
  - PN-junction leakage ( $I_{\text{junction}}$ )
  - Gate induced drain leakage ( $I_{\text{GIDL}}$ )  $\leq 65\text{nm}$
  - Depletion punch-through ( $I_{\text{punch}}$ )
- If channel is conducting:
  - Gate tunneling ( $I_{\text{gate}}$ )
  - PN-junction leakage ( $I_{\text{junction}}$ )
- If channel is switching:
  - Hot carrier injection ( $I_{\text{HCI}}$ )

 

Roy03

# Static Power

## – ITRS 2006 prognosis

 

- Subthreshold current

$$I_{sub} = I_s e^{\frac{q(V_{GS} - V_T - V_{offset})}{nkT}} (1 - e^{\frac{-qV_{DS}}{kT}})$$


- Weak inversion current
- A MOSFET operates in the weak inversion (subthreshold) region when  $V_{GS} < V_T$
- Source to drain current conduction is primarily due to diffusion of the carriers
- Subthreshold current is exponentially dependent on threshold voltage and the threshold voltage again depends on several parameters

- Simplified equation of  $V_T$  from BSIM4 manual

$$\begin{aligned}
 V_{th} = & \underbrace{V_{FB}}_{\text{Flatband Voltage}} + \underbrace{\Phi_S(T)}_{\text{Surface Potential}} + \underbrace{\gamma(\sqrt{\Phi_S + V_{bs}} - \sqrt{\Phi_S})}_{\text{Body Effect}} - \underbrace{\frac{(V_{bi}(T) - \Phi_S) + V_{ds}/2}{\cosh(L/l_c) - 1}}_{\text{Drain Induced Barrier Lowering}} \\
 & + \underbrace{\alpha(V_{bs}) \frac{\Phi_S T_{ox}}{W + \Delta W}}_{\text{Narrow Width Effect}} - \underbrace{k_{retro} V_{bs}}_{\text{Non Uniform Lateral Doping}} + \underbrace{k_{halo}(L) \sqrt{\Phi_S}}_{V_{th} \text{ Roll-up}} + \underbrace{\Delta_{DITS}(V_{ds}, T)}_{\text{Drain Induced Threshold Shift}}
 \end{aligned}$$



- First two: zero bias threshold
- Body effect
  - If bulk source voltage is 0, body effect is 0
  - A positive source voltage result in a positive term thus threshold is higher and leakage lower
- DIBL factor: the negative DIBL factor basically depends linearly on  $V_{DS}$  and exponentially on the channel length

- Drain induced barrier lowering (DIBL)
  - The depth of the junction depletion layer increases as the reverse bias voltage across the drain-to-body PN junction increases
  - Increased drain-to-body reverse bias voltage enhances the short-channel effects and lowers  $V_T$
  - Drain current is influenced by drain voltage not just gate voltage
  - A significant portion of the subthreshold leakage current of a DSM MOSFET can be due to DIBL at high reverse bias voltage across the drain-to-body PN junction

 

  
## – Gate leakage


- Tunneling: an electron on the left can pass a barrier higher than its energy with a certain probability (classically impossible)
- Tunneling current exponentially depends on barrier height  $V$  and width  $T$  and on carrier's mass  $m_{\text{eff}}$
- Leakage current can be carried by tunneling electrons or holes
  - Direct tunneling: from gate to channel
  - Fowler-Nordheim tunneling: from gate to oxide
- In the overlap region, the tunneling can carry current from the gate to source and drain directly. The current tunneling to the channel will go to source, drain or bulk



 - Maximum subthreshold leakage
  - Cut-off transistor
- Maximum gate oxide leakage
  - A transistor operates in the active region with the maximum voltage difference across the gate-to-source and the gate-to-drain terminals




Maximum subthreshold leakage

 



Maximum gate oxide leakage




- Junction leakage
  - Schematic view of a PN-junction in reverse bias
  - As known from diodes: small currents are carried by
    - Drifting carriers
    - Electron-hole generation in junction
  - As soon as built-in potential plus applied reverse bias are higher than the band gap, electrons can directly tunnel from the P-side's valence band to the N-side's conduction band → Band-To-Band-Tunneling (BTBT)

 

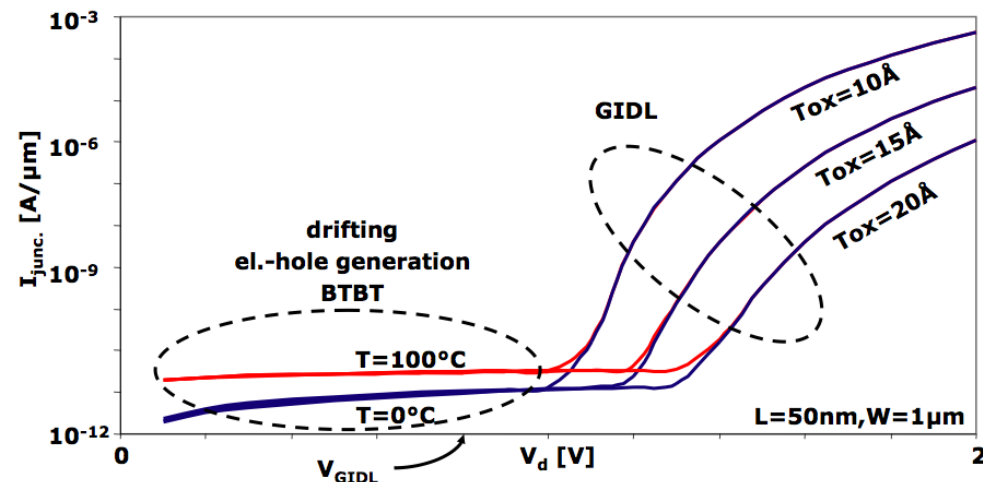 - Junction leakage
  - Smaller barrier means exponentially higher BTBT:
    - Technology scaling: steeper doping profiles
  - Gate Induced Drain Leakage (GIDL)
    - The potential difference between drain and gate makes the PN junction steeper
    - The tunneling distance smaller, and thus the current exponentially higher
  - Body biasing also influences the BTBT current



 - Depletion punch-through
  - In a sufficiently small device
  - When the drain and source depletion regions approach each other and electrically touch deep in the channel
    - Source and drain are actually merged together
  - A space-charge condition that allows the channel current to exist deep in the sub-gate region
  - Causing the gate to lose control of the sub-gate channel region



Depletion-region boundaries

- Hot carrier injection (HCI)
  - Short-channel transistors are more susceptible to the injection of hot carriers (holes and electrons) into the oxide
  - These charges are a reliability risk and are measurable as gate and substrate currents
  - Can occur in the off-state, but more typically occurs during the transistor bias states in transition

# Static Power

- Leakage power reduction
  - Lowering  $V_{DD}$  (voltage islands, dynamic voltage scaling)
  - Cooling and/or refrigeration
  - SOI technology
  - Dual  $V_T$  design
  - Body bias control (static and/or adaptive)
  - Input vector control during sleep mode
  - MTCMOS (sleep transistor)

- Two key transistor scaling schemes
  - CE (Constant electric field) scaling
    - All the horizontal and vertical dimensions are scaled with the power supply to maintain constant electric fields throughout the device
    - Standard scaling methodology in industry in a 30% reduction ( $1/S=0.7$ ) of all dimensions per generation
    - Supply and threshold voltages are scaled down by the factor of  $1/S$
    - Current, gate capacitances, and delay also scaled by  $1/S$
    - Results in  $S$  improvement in frequency
    - Improvement gradually degrades due to interconnect dominant delay
  - CV (Constant voltage) scaling
    - Maintains a constant power supply
    - Gradually scales the gate oxide thickness to slow down the growth of fields in the oxide

- CE scaling
  - Switching energy scaled down by  $1/S^3$
  - Dynamic power scaled down by  $1/S^2$
  - Operating frequency scaled up by  $S$
  - Dynamic power for a constant die size is the same
  - Number of switching elements scaled up by  $S^2$
  - Leakage power increases exponentially
- Example
  - Leakage power is 0.1% in 25um technology
  - Leakage power is 25% in 0.1um technology

# ( $V_{DD}-V_T$ ) Design Space

<i>Parameter</i>	<i>Relation</i>	<i>Full Scaling</i>	<i>General Scaling</i>	<i>Fixed-V Scaling</i>
$W, L, t_{ox}$		$1/S$	$1/S$	$1/S$
$V_{DD}, V_T$		$1/S$	$1/U$	$1$
$N_{SUB}$	$V/W_{depl}^2$	$S$	$S^2/U$	$S^2$
Area/Device	$WL$	$1/S^2$	$1/S^2$	$1/S^2$
$C_{ox}$	$1/t_{ox}$	$S$	$S$	$S$
$C_{gate}$	$C_{ox}WL$	$1/S$	$1/S$	$1/S$
$k_n, k_p$	$C_{ox}W/L$	$S$	$S$	$S$
$I_{sat}$	$C_{ox}WV$	$1/S$	$1/U$	$1$
Current density	$I_{sat}/Area$	$S$	$S^2/U$	$S^2$
$R_{on}$	$V/I_{sat}$	$1$	$1$	$1$
Intrinsic Delay	$R_{on}C_{gate}$	$1/S$	$1/S$	$1/S$
$P$	$I_{sat}V$	$1/S^2$	$1/U^2$	$1$
Power density	$P/Area$	$1$	$S^2/U^2$	$S^2$

[http://www.csee.umbc.edu/~cpatel2/links/640/lectures/lect11\\_scaling.pdf](http://www.csee.umbc.edu/~cpatel2/links/640/lectures/lect11_scaling.pdf)



- Simple hand calculation model that empirically fits the real data

$$I_{DS} = K_S \frac{W}{L} (V_{GS} - V_T)^\alpha$$

Measured data (pointing to  $K_S$ )

Measured data (pointing to  $\alpha$ )

$$I_{ON} = I_0 (S\alpha)^{-\alpha} (V_{GS} - V_T)^\alpha$$

- $\alpha$  is close to 1 than 2, which is approximately 1.25, and continue to approach to 1 as technology scales

$$I_{sub} = I_0 e^{-\alpha} e^{\frac{V_{GS} - V_T}{S}}$$

$$\text{Delay} \propto \frac{V_{DD}}{(V_{DD} - V_T)^\alpha}$$

- $(V_{DD}-V_T)$  design space

- Delay of a gate

$$t_{pd} \propto \frac{C_L V_{DD}}{(V_{DD} - V_T)^\alpha} \quad \leftarrow \text{Short-channel effect}$$

- Subthreshold leakage current increases exponentially as  $V_T$  decreases

$$I_{sub} = I_S e^{\frac{-|V_T| \ln 10}{S}}$$

- For a given process and  $V_{DD}/V_T$  ratio, the energy efficient  $V_T$  point is significantly below the typical threshold levels of today's technology
  - Excessive headroom for  $(V_{DD}-V_T)$  scaling
  - But lowering  $V_T$  results in bad noise margin, short-channel effect, and  $V_T$  variation

- Power minimization in both active and standby modes
  - Dynamic power in active mode
  - Subthreshold leakage power in standby mode

- Slides are modified from lecture notes of “Advanced Computer System Design” from Seoul National University (Lecturer: Prof. Naehyuck Chang)